

MODEL PAPER  
B.Sc ( Three year ) Degree Examinations.  
**SEMISTER-III ELECTRONICS**  
Paper-III DIGITAL ELECTRONICS

Time: 3 Hrs

MaxMarks:75

**PART-A**

Answer any FIVE Questions

5x5 =25Marks.

1. (a) Convert  $(3A.2F)_{16}$  in to decimal.  
(b) Convert  $(1011.111)_2$  to Octal.
2. Give NOR gate implementation for OR,AND and NOT gates?
3. Simplify the Boolean expressions.

$$(i) Y = A B C + A \bar{B} + A B \bar{C}$$

$$(ii) Y = A C D + \bar{A} B C D$$

4. Discuss the working of parallel Binary Adder?
5. Explain the working of a 4 : 1 line multiplexer with the help of logic diagram?
6. Describe the working of D Flip-Flop. How it is obtained from the JK Flip-Flop?
7. Draw the logic diagram for 4-bit SIPO shift register and explain its working?
8. How does the architecture of PLA differ from PAL and PROM?

**PART-B**

Answer ALL Questions

10X5 =50marks.

9. a) Discuss in detail about Binary, Decimal and Hexadecimal number systems. What are the advantages of Decimal and Hex systems over Binary?  
( OR )  
b) What is Gray code. Write Gray code for any 4-bit binary number. Give the advantage of Gray code over binary System.
10. a) Discuss about the postulates and theorems of Boolean Algebra?  
( OR )  
b) Reduce the following expression using K-map and implement in universal logic?  
 $\sum m(0,1,4,5,6,7,9,11,15)+d(10,14)$
11. a) Explain the working of Half adder and Full adder with the help of logic diagrams and truth tables?  
( OR )  
b) Explain the working of TTL NAND gate and CMOS NOR gate?
12. a) Explain the working of Master – Slave JK Flip-Flop .How Race Condition is eliminated in it?  
(OR)  
b) With the help of logic diagram explain the working of 3- bit asynchronous UP/DOWN Counter?
13. a) Draw the Block diagram of PLA and explain about each stage?  
( OR )  
b) A 3-input,4-output combinational circuit has the following output functions.  
Implement the Circuit  
 $A(x,y,z)=\sum m(1,2,4,6)$   $B(x,y,z)=\sum m(0,1,3,6,7)$   $C(x,y,z)=\sum m(1,2,4,6,7)$   
 $D(x,y,z)=\sum m(1,2,3,5,7)$

MODEL PAPER  
B.Sc ( Three year ) Degree Examinations.  
**SEMISTER-IV ELECTRONICS**  
Paper-IV ANALOG& DIGITAL I.C APPLICATIONS

Time: 3 Hrs

MaxMarks:75

**PART-A**

Answer any FIVE Questions

5x5=25Marks.

- 1.Explain the concept of virtual ground in OP-AMP?
- 2.Define slew rate of OP-AMP and derive slew rate expression for sinusoidal input?
- 3.Describe the working of inverting comparator using OP-AMP?
- 4.Draw OP-AMP Integrater circuit and explain how it works?
- 5.With the help of logic diagram explain about Binary-to-Gray code converter?
- 6.Explain the working of 4-bit synchronous counter and give its timing diagram?
- 7.Write about the specifications that help in selecting an A/D converter?
- 8.Explain how a shift register can be used as an UART?

**PART-B**

Answer ALL Questions

10X5 =50 marks.

- 9.a)With a neat circuit diagram explain the working of R-2R ladder type D/A converter?

(OR)

- b)Give a detailed explanation on the working of successive approximation A/D converter?

- 10.a)Draw the OP-AMP inverting & non-inverting amplifier configurations.Explain their working and obtain expressions for gain?

(OR)

- b)Draw the pin diagram of IC555 timer and explain function of each pin?

- 11.a)Give the circuit for OP-AMP triangular wave form generator.Explain its operation and obtain expression for frequency of triangular output?

(OR)

- b)Describe the working of IC555 in Astable mode. Obtain expression for frequency of oscillations?

12.a) Design Binary-to-BCD code converter using K-map reduction method. Give its logic diagram?

(OR)

b) With the help of J-K FF excitation table, design a synchronous Mod-5 counter?

13.a) With simplified logic diagram describe the operation of Digital clock?

(OR)

b) Explain how shift register works as serial to parallel and parallel to serial converter?

## **B.Sc- ELECTRONICS PRACTICALS**

### **SCHEME OF VALUATION FOR ALL SEMESTERS**

- 1.Principle/Statement -----2marks
- 2.Circuit diagram with component labelling-----5marks
- 3.Tabularform/Formula/Modelgraph-----  
6marks(3+2+1)
- 4.Observations-----12marks
- 5.Calculations/Graph/Result-----  
10marks(5+3+2)
- 6.Viva-----5marks
- 7.Record-----10marks

TOTAL= 50marks